

# **Hardware Design and Lab: Lab4**

**111060013 EECS 26' 劉祐廷**

# Catalog

## 1. Basic Question:

**Many-to-one LFSR and One-to-many LFSR.....P3**

## 2. Advanced Question:

**Content-addressable memory (CAM) design.....P4**

## 3. Advanced Question:

**Scan Chain Design.....P6**

## 4. Advanced Question:

**Built-in Self Test.....P8**

## 5. Advanced Question:

**Built-in Self Test FPGA.....P10**

**6. What I Have Learned.....P15**

# 1. Basic Question

## A. Many-to-one LFSR

### I. State Transition Diagram

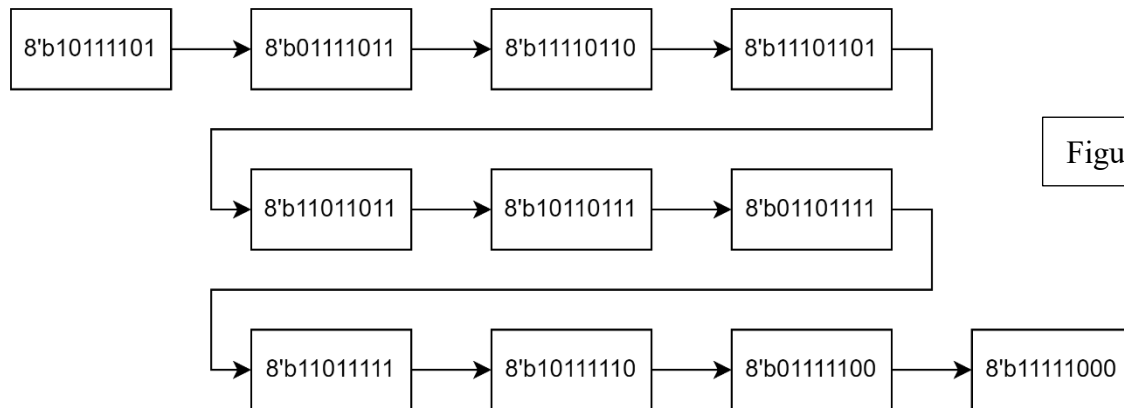


Figure 1.1

### II. Basic Question

If we reset the DFFs to 8'd0, then DFFs will remain 8'd0 because  $(DFF[1] \wedge DFF[2]) \wedge (DFF[3] \wedge DFF[7])$  is 0. Therefore, out will be a constant 1'b0.

## B. One-to-many LFSR

### I. State Transition Diagram

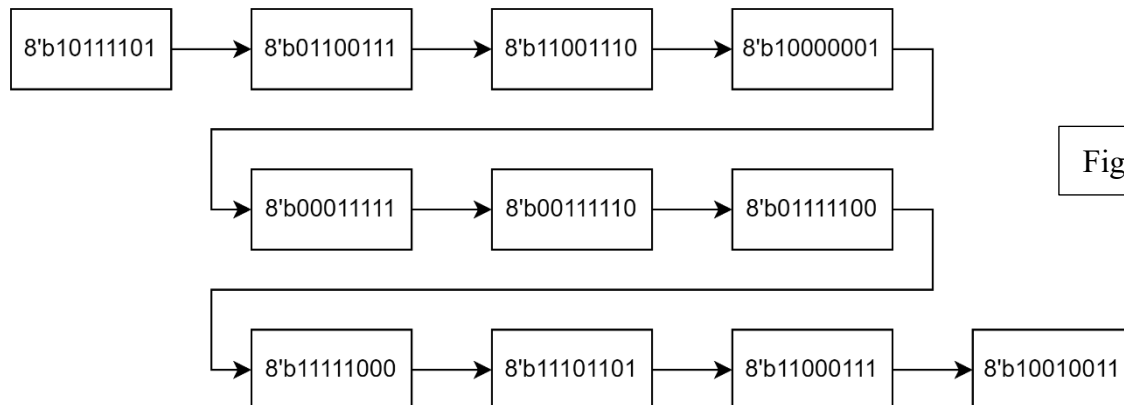


Figure 1.2

### II. Basic Question

If we reset the DFFs to 8'd0, then DFFs will remain 8'd0 because  $DFF[7] \text{ XOR any other bit}$  is 0. Therefore, out will be a constant 1'b0.

## 2. Advanced Question: Content-addressable memory (CAM) design

### A. Block Diagram

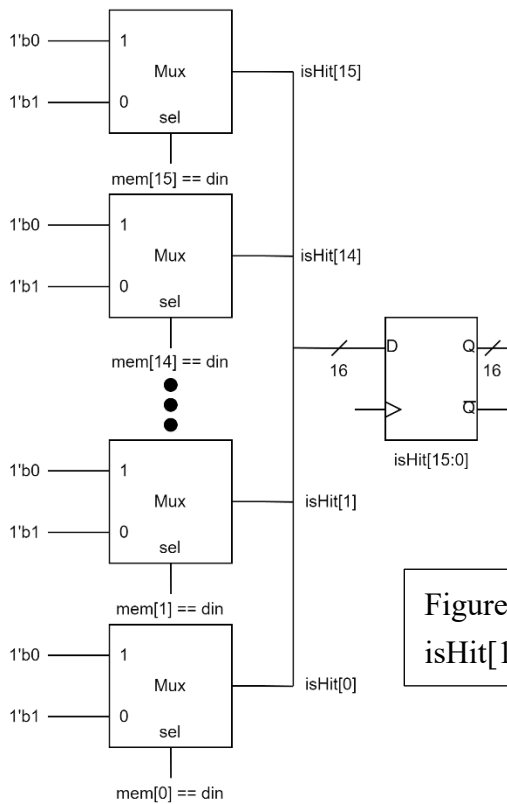


Figure 2.1  
isHit[15:0]

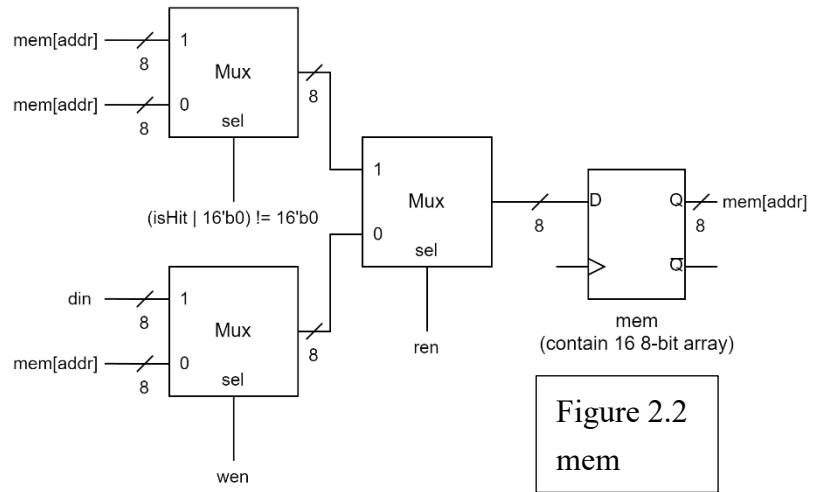


Figure 2.2  
mem

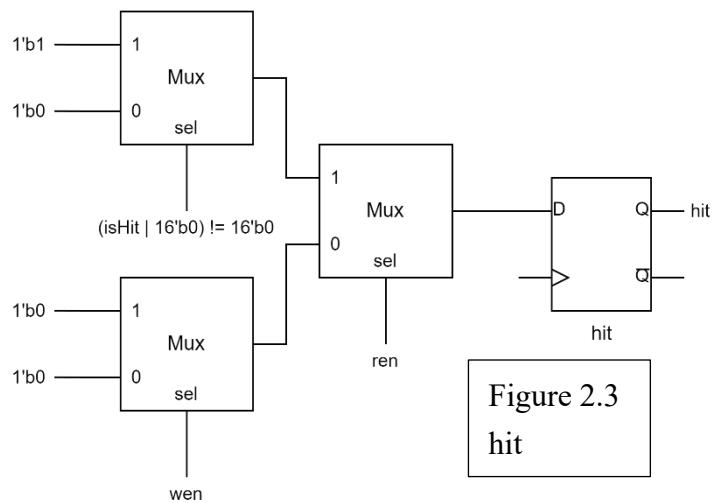


Figure 2.3  
hit


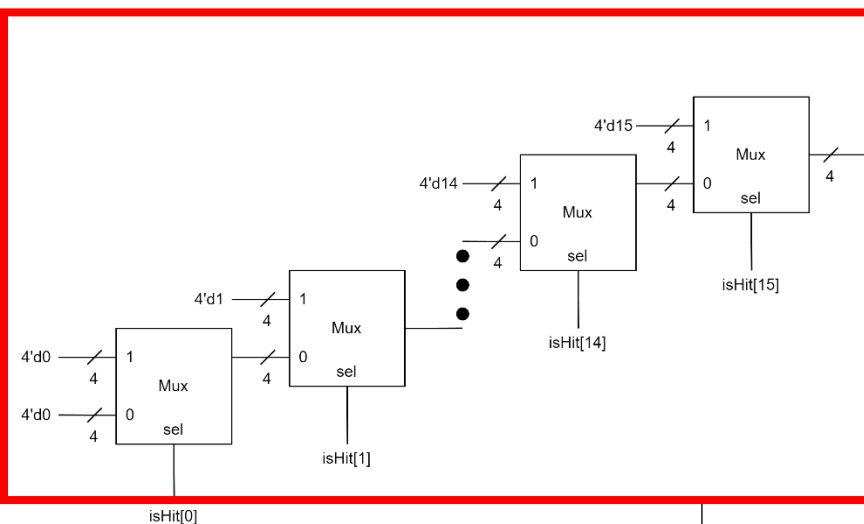


Figure 2.4  
dout

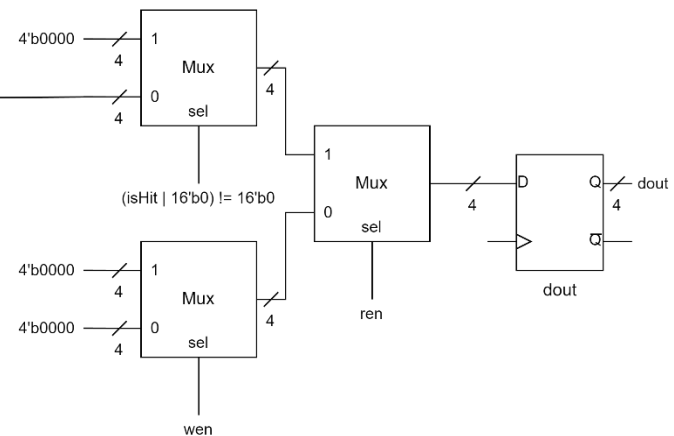

## B. Explanation

In this problem, I defined a reg called **isHit[15:0]** as **Figure 2.1** to save the hit status. If the *i*-th bit in **isHit** equal to **din**, then **isHit[i]** will be set to 1'b1. Otherwise it will be set to 1'b0. **Figure 2.2** shows how I design the memory. If **ren** is 1'b0 and **wen** is 1'b1, then **din** will be written into **mem[addr]**. Otherwise, **mem[addr]** will not change. As mention above, **isHit == 16'b0** means that there is no hit condition happened. Therefore, I designed **hit** as it shows in **Figure 2.3**. According to the specification, if **hit == 1'b1**, we should output the largest address of the bits that is hit. So I designed the circuit as it shows in **Figure 2.4** to realize this function.

## C. Testbench

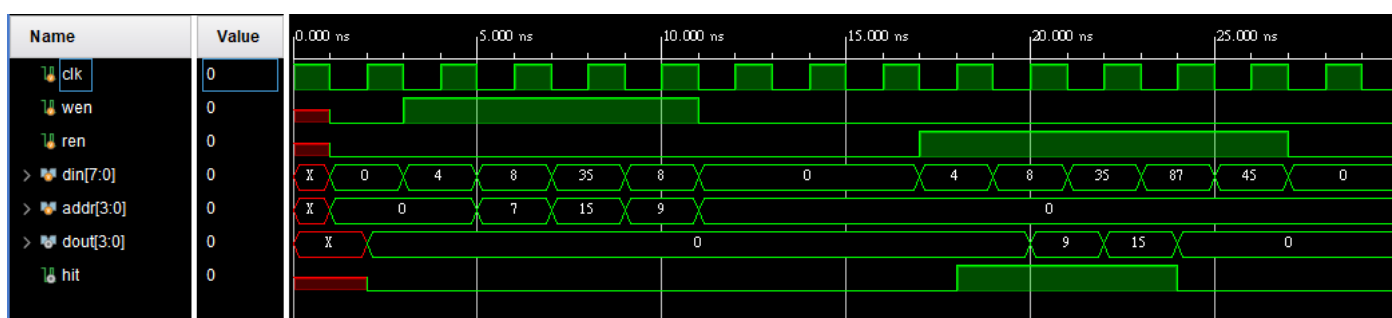


Figure 2.5 wave form 1

First, I use the input data from lecture slide to test if there is something wrong or not. As the result showed in **Figure 2.5**, we can see that everything works correctly. And then I also add some extra testcases to check if the design work correctly. As **Figure 2.6** shows, it seems that it works correctly.

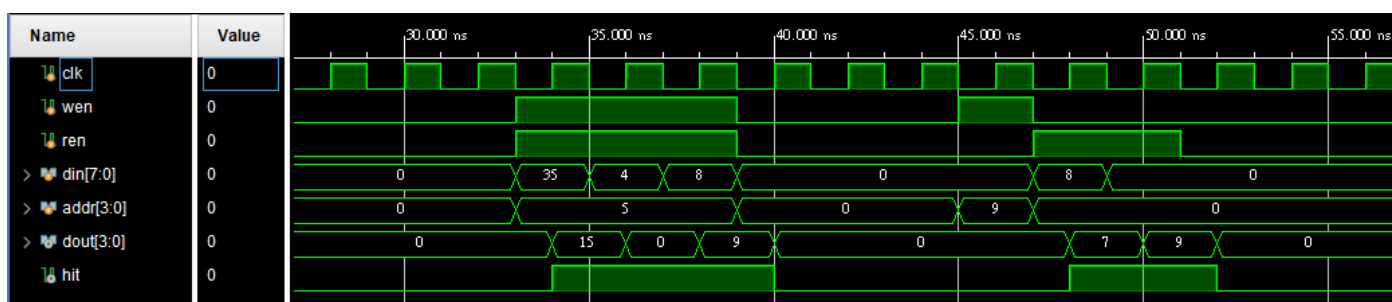


Figure 2.6 wave form 2

### 3. Advanced Question: Scan Chain Design

#### A. Block Diagram

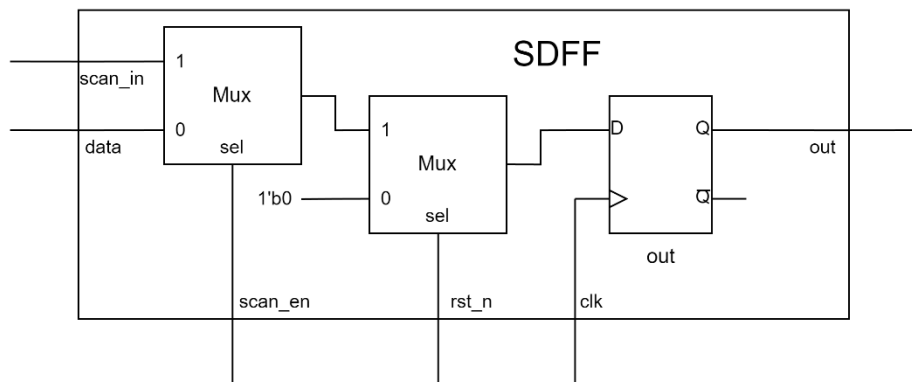


Figure 3.1  
SDFF

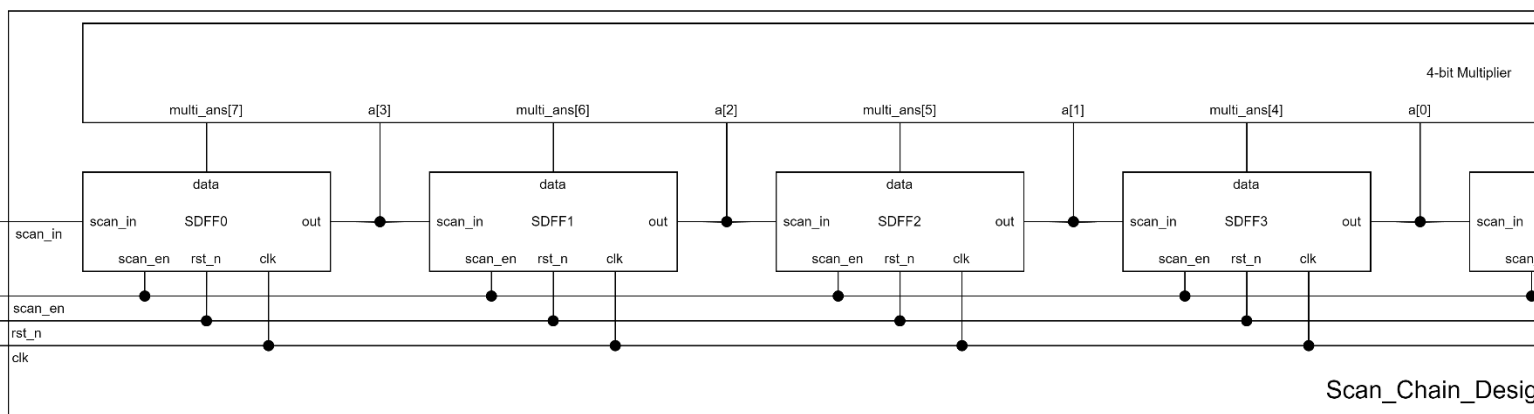


Figure 3.2  
Scan\_Chain\_Design (Left Part)

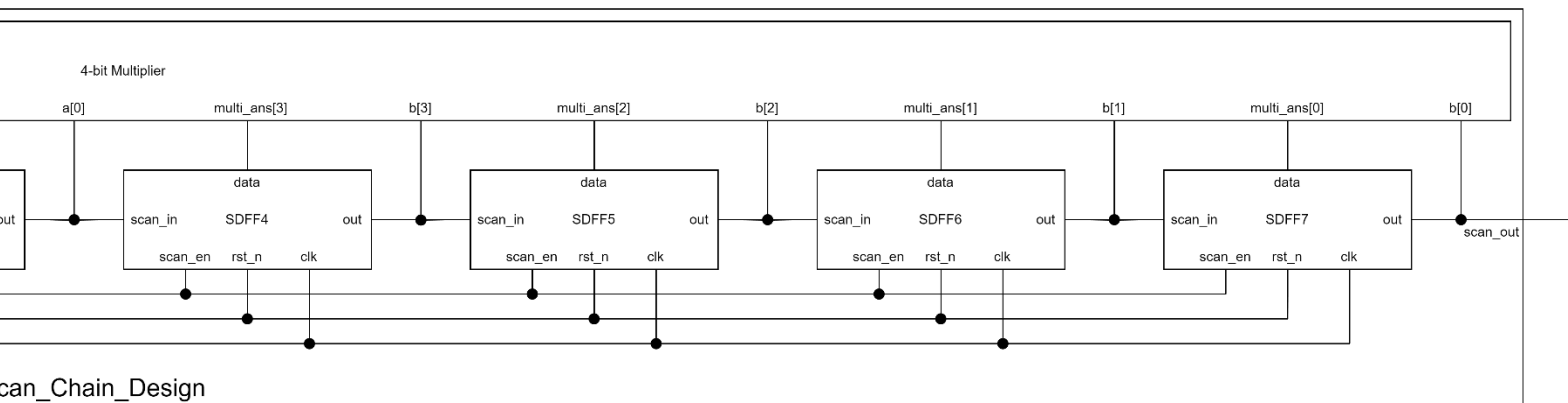


Figure 3.3  
Scan\_Chain\_Design (Right Part)

## B. Explanation

In this problem, the lecture slides provide a complete design. Thus I realize the circuit by Verilog according to the **Figure 3.1**, **Figure 3.2**, and **Figure 3.3**. Note that **4-bit Multiplier** is designed by behavioral-level code.

## C. Testbench

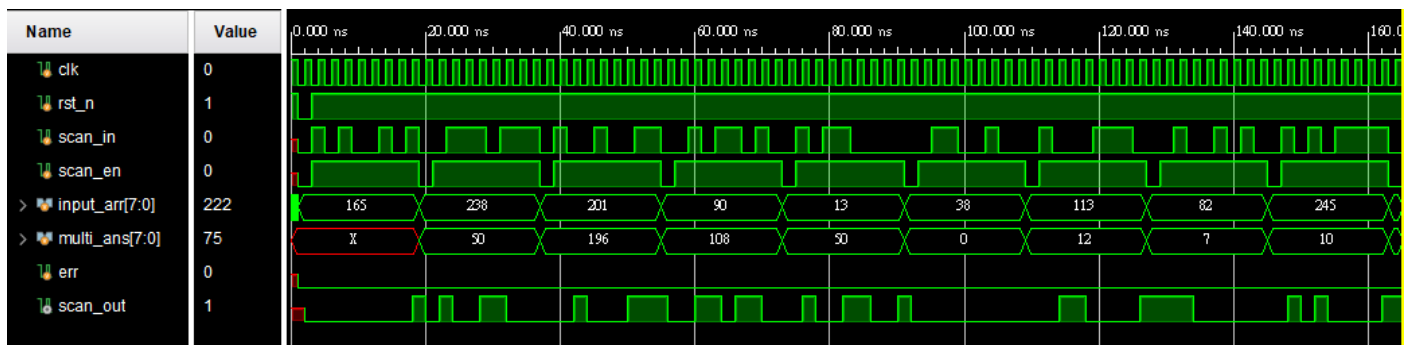


Figure 3.4  
Wave form

In this problem, I found that it is difficult to judge the results with the naked eyes. Therefore, as I've learned from Lab2, I defined a signal called **err** to help me check the result. In testbench, the input sequence will be stored in **input\_arr[7:0]** first. And then it will be scan bit by bit into the DFFs. After input 8 bits of data, it will count **multi\_ans[7:0]** as **input\_arr[7:4] \* input\_arr[3:0]** and then **input\_arr** will be set to the next testcase. After **scan\_en** pulled up again, the testbench will check the output bit by bit compare to **multi\_ans**. If detecting any errors, **err** will be pulled up. Note that **err** will be reset to 1'b0 while **scan\_en** is 1'b0. In this way, I can check the output more efficiently and precisely.

## 4. Advanced Question: Built-in Self Test

### A. Block Diagram

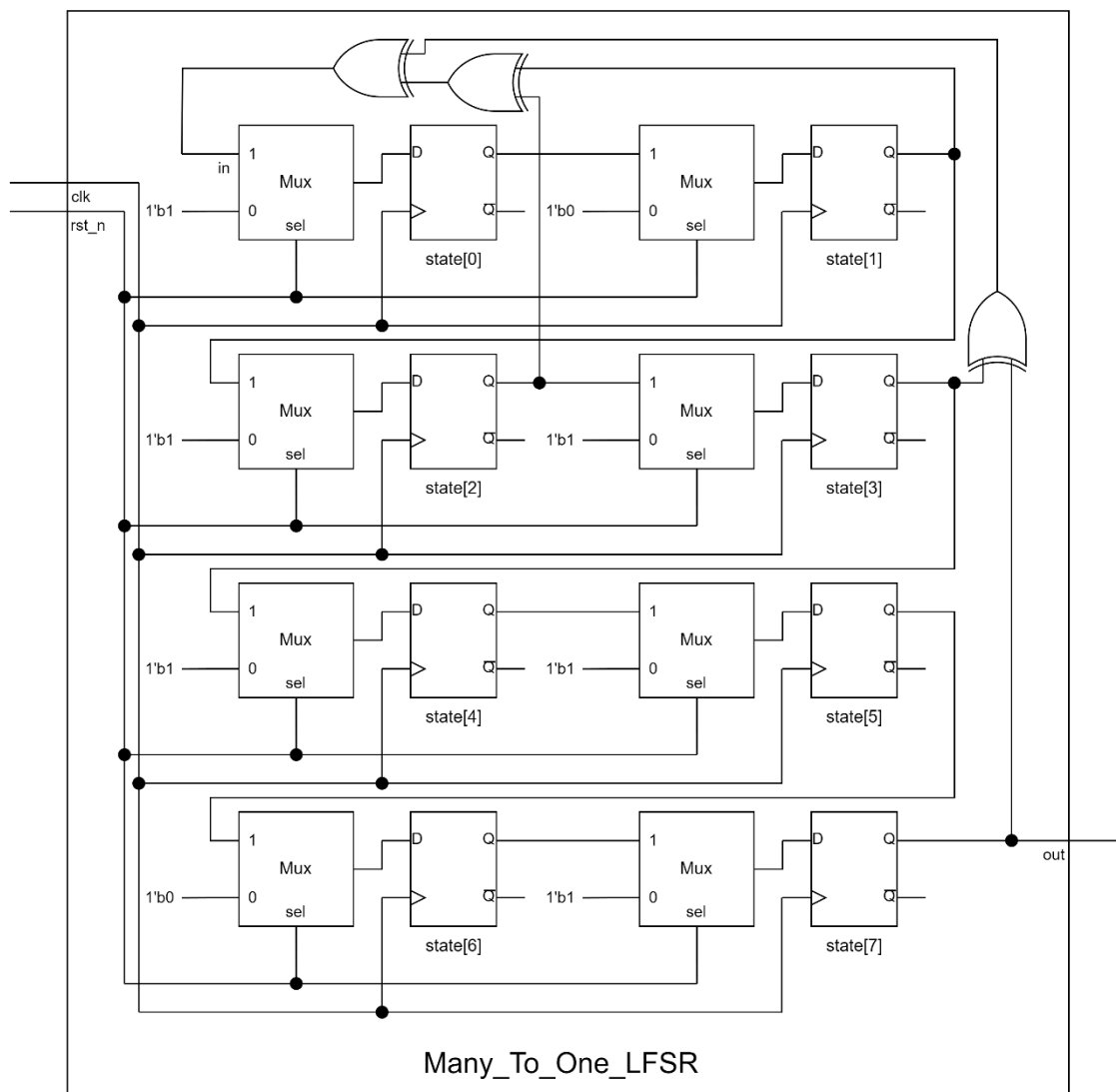


Figure 4.1 Many\_To\_One\_LFSR

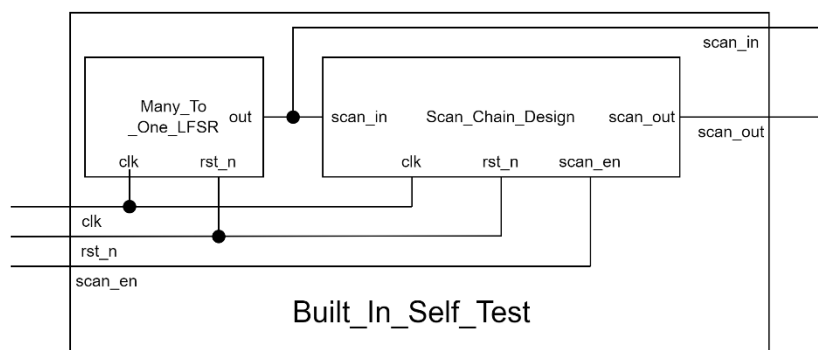


Figure 4.2 Built\_In\_Self\_Test



## B. Explanation

In this problem, I only have to combine to modules I've designed in the previous problems. **Figure 4.1** shows how I designed **Many\_To\_One\_LFSR**. **Figure 4.2** shows how I connect these two modules together.

## C. Testbench

 


Figure 4.3 wave form

In this design, testcases are generated by **Many\_To\_One\_LFSR**. It seems that the method of how I designed in the testbench of **Scan\_Chain\_Design** is risky because there are some chances that I have some wrong cases in my testbench. Therefore, I write a code in C++ to simulate the testcases and check the results one by one. And every result seems right.

```

1  #include <iostream>
2
3  #define N 16
4
5  int main() {
6      int arr[8] = {1, 0, 1, 1, 1, 1, 0, 1};
7      for (int i = 0; i < N ; i++) {
8          std::cout << i << ": ";
9          for (int j = 7; j >= 0; j--) std::cout << arr[j];
10         std::cout << '\n';
11         int tmp1 = arr[1] ^ arr[2];
12         int tmp2 = arr[3] ^ arr[7];
13         int in = tmp1 ^ tmp2;
14         for (int j = 7; j >= 1; j--) arr[j] = arr[j - 1];
15         arr[0] = in;
16     }
17     std::cout << N << ": ";
18     for (int j = 7; j >= 0; j--) std::cout << arr[j];
19     std::cout << '\n';
20 }
```

Figure 4.4

C++ code for simulating the testcases

## 5. Advanced Question: Built-in Self Test FPGA

### A. Block Diagram

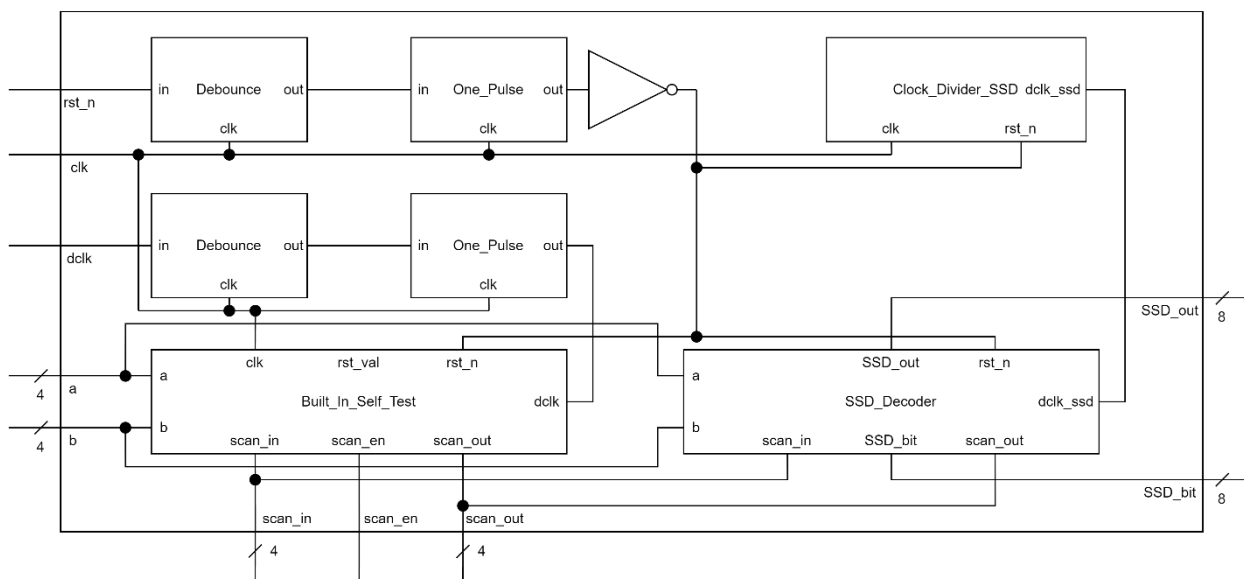


Figure 5.1  
The whole design of this problem

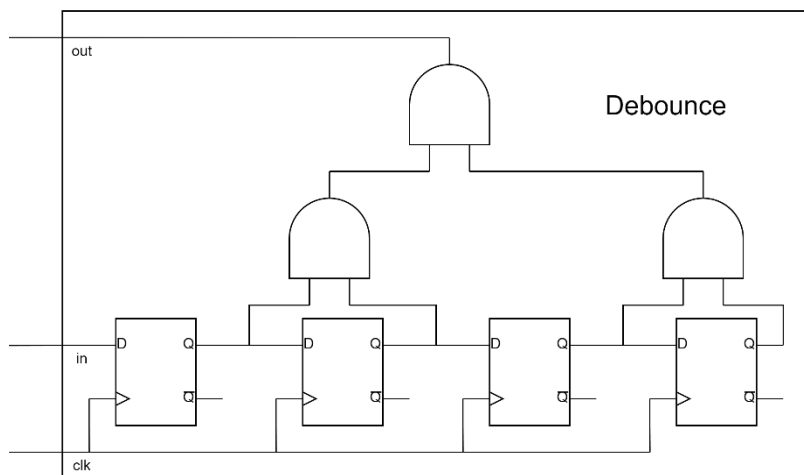


Figure 5.2  
Debounce


 
 
 


Figure 5.3  
One\_Pulse

 

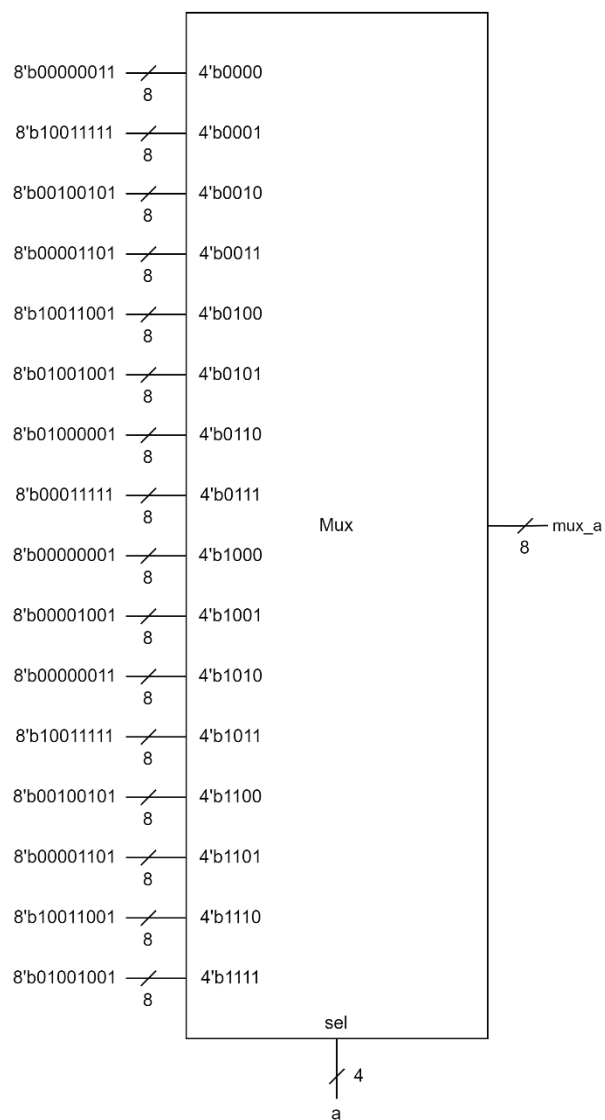


Figure 5.7  
mux\_a

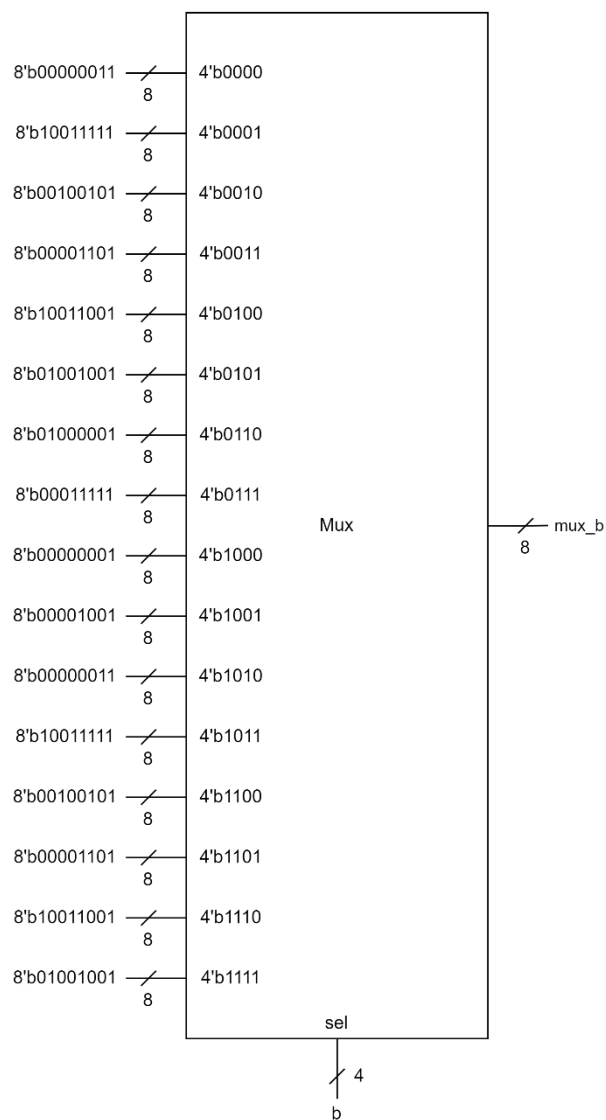


Figure 5.8  
mux\_b

 


Figure 5.9  
mux\_in

 


Figure 5.10  
mux\_out

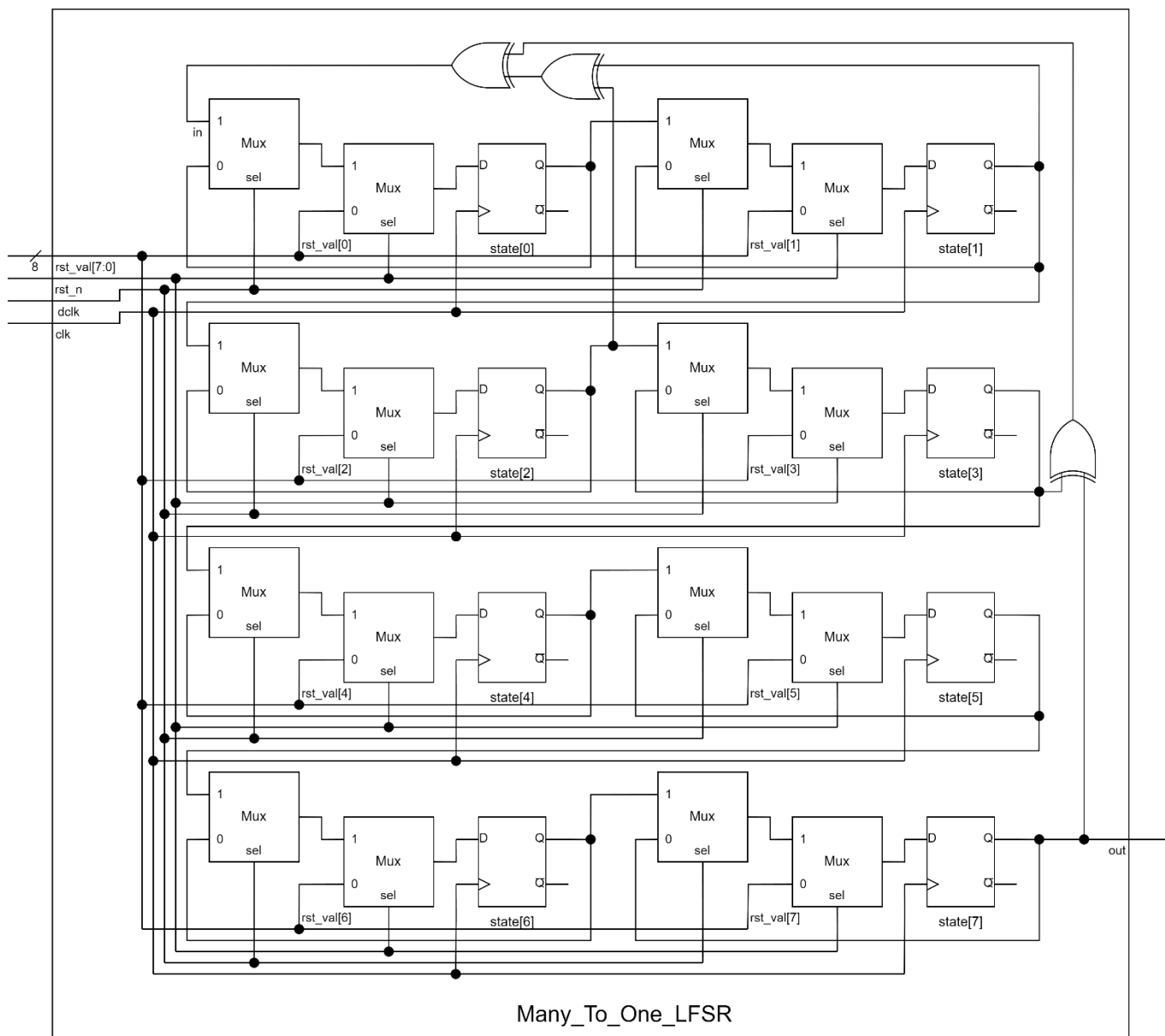


Figure 5.11  
Many\_To\_One\_LFSR

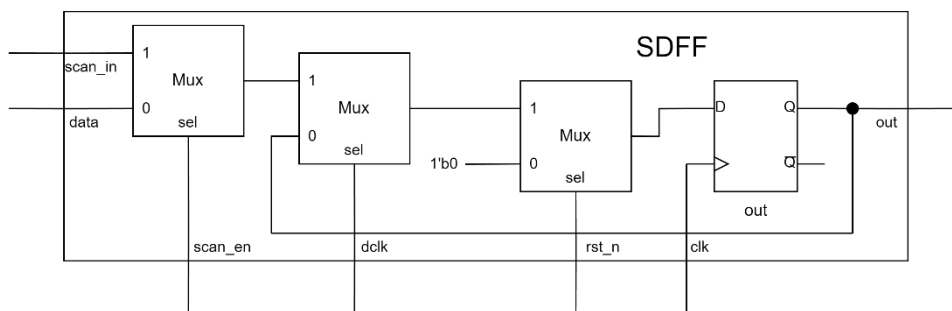


Figure 5.12  
SDFF

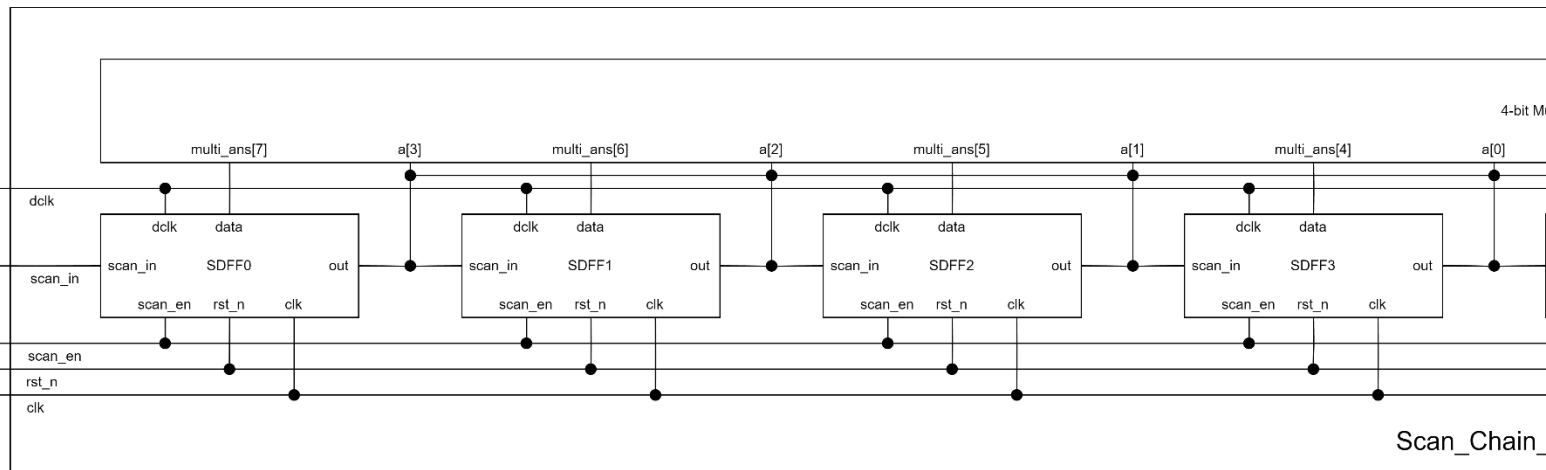


Figure 5.13  
Scan\_Chain\_Design (Left Part)

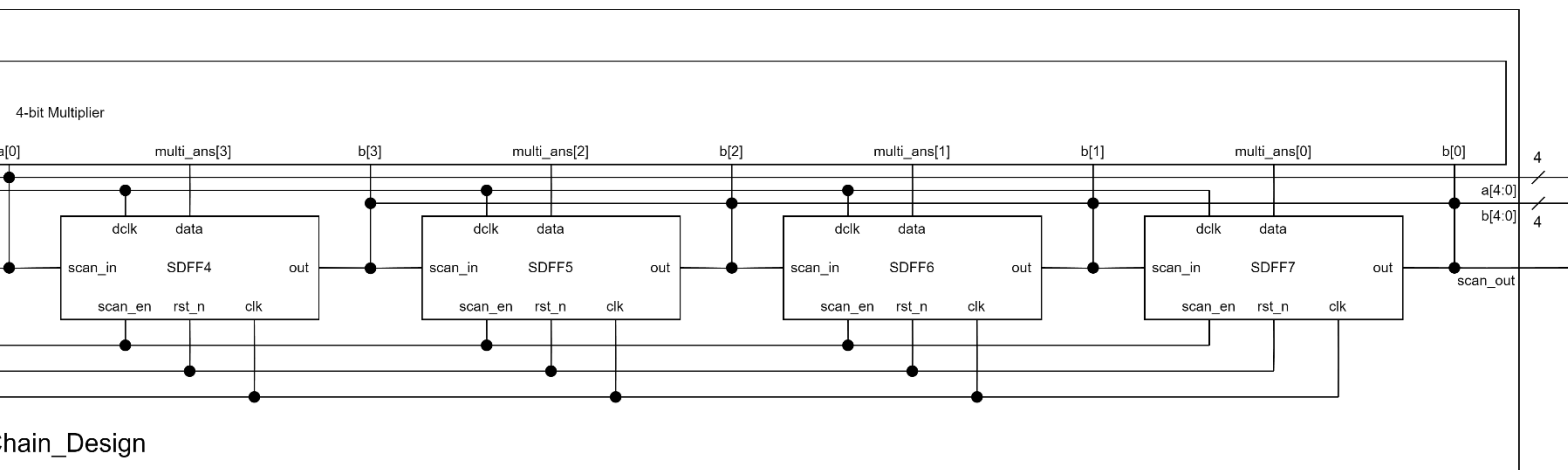


Figure 5.14  
Scan\_Chain\_Design (Left Part)

## B. Explanation

According to the specification, I divided the circuit into different modules as **Figure 5.1** shows. In order to work properly on FPGA boards, divided clock is needed. Most of the modules above are modified from the designs of the previous problems by adding a mux which selected by **dclk** before connect into DFFs. However, after testing on the FPGA board, I noticed that there is some chance that the DFFs will go through two states while I only press the button one time. To solve this problem, I use a divided clock to control **Debounce** module as **Figure 5.15** shows. In this way, it seems the condition mentioned above doesn't happen again while I was testing it on the FPGA board.

```
always @ (posedge clk) begin
    if (dclk_db) DFF <= {DFF[2:0], in};
    else DFF <= DFF;
end
```

Figure 5.15

## 6. What I Have Learned

Most of modules are provided in the lecture slides, thus I spent much less time designing modules. However, it is difficult to design a testbench in this lab. In order to check the results, I used the method that I've learned from Lab2 and also wrote a C++ program to generate testcases correctly to help me debug. In this lab, I've learned that how to combined the skills that I've learned before to solve problems. I hope that I can use these skills more flexible in the future.